

## Chapter.7 Alternating Current Class – XII Subject – Physics

- 7.1.** A  $100\ \Omega$  resistor is connected to a 220 V, 50 Hz ac supply.
- What is the rms value of current in the circuit?
  - What is the net power consumed over a full cycle?

**Sol.**

Given:

$$R = 100\ \text{ohms}$$

$$V = 220\ \text{V}$$

$$f = 50\ \text{Hz}$$

- a) We know

$$I_{\text{rms}} = V_{\text{rms}} / R$$

Substituting the values

$$I_{\text{rms}} = 220 / 100 = 2.2\ \text{A}$$

- b) Power =  $V.I$

$$\text{Or Power} = 220 \times 2.2$$

$$\text{Or Power} = 484\ \text{W}$$

**7.2.**

- The peak voltage of an ac supply is 300 V. What is the rms voltage?
- The rms value of current in an ac circuit is 10 A. What is the peak current?

**Sol.**

a) We know

$$V_{rms} = V_{peak} / 1.414$$

$$V_{rms} = 300 / 1.414$$

$$\text{Or } V_{rms} = 212.13 \text{ V}$$

b) Using above identity for current

$$I_{peak} = 1.414 \times I_{rms}$$

$$\text{Or } I_{peak} = 1.414 \times 10 = 14.14 \text{ A}$$

**7.3.** A 44 mH inductor is connected to 220 V, 50 Hz ac supply. Determine the rms value of the current in the circuit.

**Sol.**

Given:

$$L = 44 \text{ mH}$$

$$V = 220 \text{ V}$$

$$f = 50 \text{ Hz}$$

$I_{rms}$  is given by  $= V / X_L$

Determining inductive reactance

$$X_L = 2 \times 3.14 \times 50 \times 44 \times 10^{-3}$$

$$X_L = 13.82 \text{ ohms}$$

Therefore

$$I_{rms} = 220 / 13.82$$

$$\text{Or } I_{rms} = 15.92 \text{ A}$$

**7.4.** A 60  $\mu\text{F}$  capacitor is connected to a 110 V, 60 Hz ac supply. Determine the rms value of the current in the circuit.

**Sol.**

Given:



$C = 60$  microfarads

$V = 110$  volts

$f = 60$  hertz

$$I_{rms} = V / X_c$$

Now

$$X_c = 1 / (2 \times 3.14 \times 60 \times 60 \times 10^{-6})$$

$$X_c = 44.248 \text{ ohms}$$

Hence

$$I_{rms} = 110 / 44.248 = 2.488 \text{ A}$$

**7.5.** In Exercises 7.3 and 7.4, what is the net power absorbed by each circuit over a complete cycle. Explain your answer.

**Sol.**

Zero. Power is absorbed only by resistance in the circuit.

**7.6.** Obtain the resonant frequency  $\omega_r$  of a series LCR circuit with  $L = 2.0\text{H}$ ,  $C = 32 \mu\text{F}$  and  $R = 10 \Omega$ . What is the Q-value of this circuit?

**Sol.**

Given:

$$L = 2 \text{ H}$$

$$C = 32 \text{ microF}$$

$$R = 10 \text{ ohms}$$

$$\text{Resonant frequency } \omega_r = \frac{1}{\sqrt{LC}}$$

Substitution yields

$$\omega_r = 125 \text{ /s}$$

Now Q-value =  $\omega_r L / R$

Putting the desired values gives us

Q-value = 25

- 7.7.** A charged 30  $\mu\text{F}$  capacitor is connected to a 27 mH inductor. What is the angular frequency of free oscillations of the circuit?

**Sol.**

Given:

$C = 30 \text{ microF}$

$L = 27 \text{ mH}$

Angular frequency of free oscillations =  $\frac{1}{\sqrt{LC}}$

Substitution results

Angular frequency = 1111.11 /s

- 7.8.** Suppose the initial charge on the capacitor in Exercise 7.7 is 6 mC. What is the total energy stored in the circuit initially? What is the total energy at later time?

**Sol.**

Initial energy,  $U_i = q_m^2 / 2C$

Solving

$U_i = 0.6 \text{ J}$

The energy will remain constant at all times.



- 7.9.** A series LCR circuit with  $R = 20\ \Omega$ ,  $L = 1.5\ \text{H}$  and  $C = 35\ \mu\text{F}$  is connected to a variable-frequency  $200\ \text{V}$  ac supply. When the frequency of the supply equals the natural frequency of the circuit, what is the average power transferred to the circuit in one complete cycle?

**Sol.**

Given:

$$R = 20\ \text{ohms}$$

$$L = 1.5\ \text{henries}$$

$$C = 35\ \text{micro farads}$$

$$V = 200\ \text{volts}$$

Natural frequency

$$\begin{aligned} &= \frac{1}{\sqrt{LC}} \\ &= 138\ \text{/s} \end{aligned}$$

At natural frequency,

$$Z = R$$

$$\text{So } I = V / R = 200 / 20 = 10\ \text{A}$$

Thus

$$P = I^2 R$$

$$\text{Or } P = 10 \times 10 \times 20 = 2000\ \text{W}$$

- 7.10.** A radio can tune over the frequency range of a portion of MW broadcast band: (800 kHz to 1200 kHz). If its LC circuit has an effective inductance of  $200\ \mu\text{H}$ , what must be the range of its variable capacitor? [Hint: For tuning, the natural frequency i.e., the frequency of free oscillations of the LC circuit should be equal to the frequency of the radio wave.]

**Sol.**

By the relation

$$\frac{1}{\sqrt{LC}} = 2\pi f$$

Solving for C

$$C = \frac{1}{4\pi^2 f^2 L}$$

For  $f = 800 \text{ kHz}$ ,


$$C' = 197.8 \text{ pF}$$

For  $f = 1200 \text{ kHz}$ ,

$$C'' = 87.9 \text{ pF}$$

Range: 88 pF to 198 pF

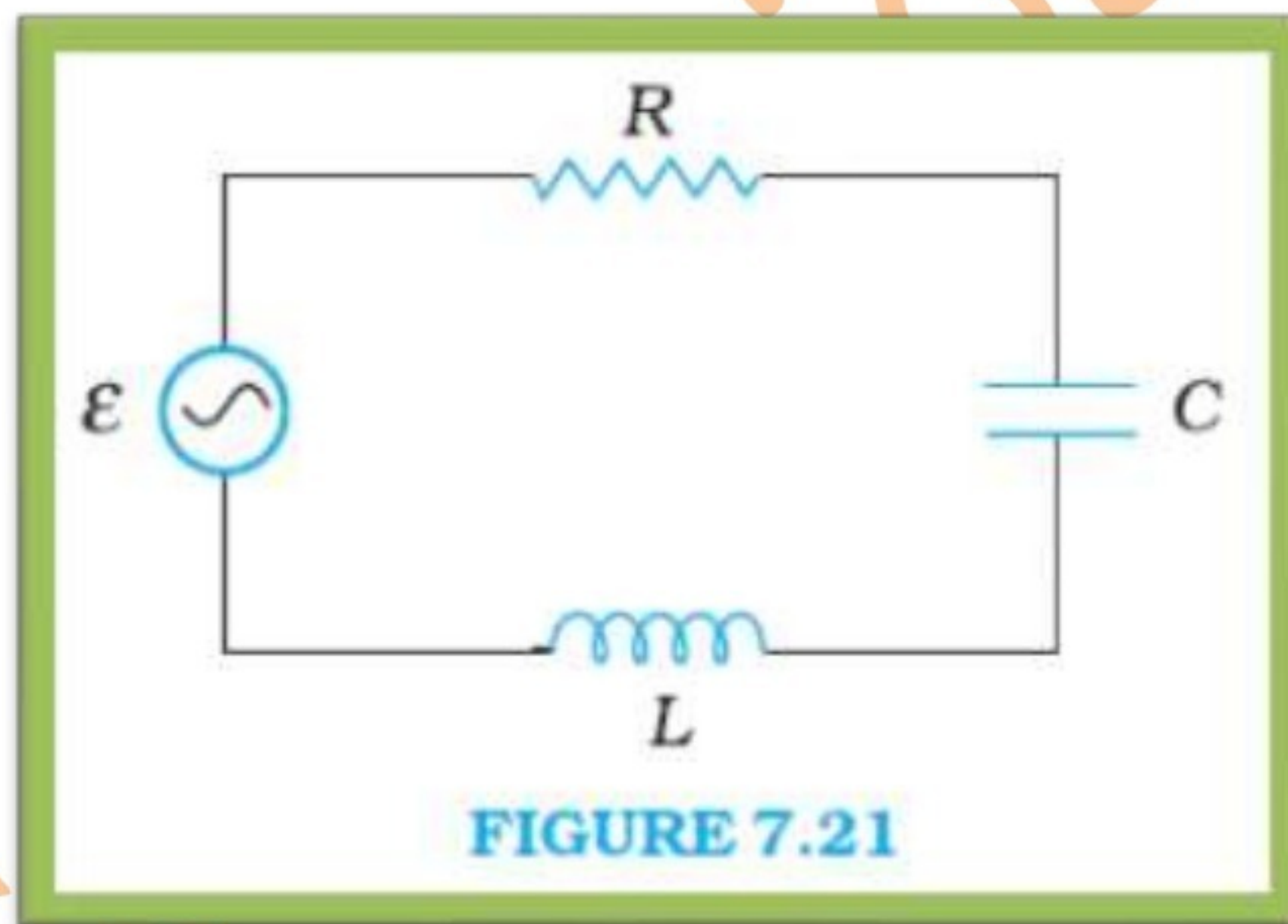**7.11.** Figure 7.21 shows a series LCR circuit connected to a variable frequency 230 V source.  $L = 5.0 \text{ H}$ ,  $C = 80 \mu\text{F}$ ,  $R = 40 \Omega$ .



- Determine the source frequency which drives the circuit in resonance.
- Obtain the impedance of the circuit and the amplitude of current at the resonating frequency.
- Determine the rms potential drops across the three elements of the circuit. Show that the potential drop across the LC combination is zero at the resonating frequency.



**Sol.**

Given:

$$V = 230 \text{ V}$$

$$L = 5 \text{ H}$$

$$C = 80 \mu\text{F}$$

$$R = 40 \text{ ohms}$$

a) Source frequency at resonance  $= \frac{1}{\sqrt{LC}}$

Solving by putting respective values  
 $= 50 \text{ rad / s}$

b) At resonance,

$$\text{Impedance, } Z = \text{Resistance, } R$$

$$\text{So } Z = R = 40 \text{ ohms}$$

Now rms value of current,

$$I = V / R$$

$$\text{Or } I = 230 / 40$$

$$\text{Hence } I = 5.75 \text{ A}$$

$$\begin{aligned} \text{Amplitude of this value of current} &= 1.414 \times I \\ &= 1.414 \times 5.75 \\ &= 8.13 \text{ A} \end{aligned}$$

c) Now taking into consideration the rms potential drops

Across Resistance

$$\begin{aligned} V_R &= IR \\ &= 5.75 \times 40 \\ &= 230 \text{ V} \end{aligned}$$

Across Capacitance

$$\begin{aligned} V_C &= IX_C \\ &= 1437.5 \text{ V} \end{aligned}$$

Across Inductance

$$\begin{aligned} V_L &= IX_L \\ &= 5.75 \times 50 \times 5 \\ &= 1437.5 \text{ V} \end{aligned}$$

Across LC combination

$$\begin{aligned}V_{LC} &= I(X_L - X_C) \\ &= 0 \text{ (at resonating frequency)}\end{aligned}$$

Hence shown!

cbse.jagranjosh.com